

VHDL Moore FSMs

Agostini Federico

1 Code of break_measure.vhd architecture

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  -- Uncomment the following library declaration if using
5  -- arithmetic functions with Signed or Unsigned values
6  use IEEE.NUMERIC_STD.ALL;
7
8  -- Uncomment the following library declaration if instantiating
9  -- any Xilinx leaf cells in this code.
10 --library UNISIM;
11 --use UNISIM.VComponents.all;
12
13 entity break_measure is
14     generic(DONE_TIME : integer := 100);
15     Port (clk      : in  std_logic;
16          rst      : in  std_logic;
17          pulses_in : in  std_logic;           -- Counter input
18          count_out : out unsigned(5 downto 0); -- break time measurement in clock cycles
19          done_out  : out std_logic);          -- Calculation done
20 end break_measure;
21
22 architecture Behavioral of break_measure is
23
24     -----
25     ----- WRITE YOUR CODE HERE -----
26     -----
27 COMPONENT ila_1
28 PORT (
29     clk : IN STD_LOGIC;
30     probe0 : IN STD_LOGIC_VECTOR(0 DOWNTO 0); -- pulses_in
31     probe1 : IN STD_LOGIC_VECTOR(0 DOWNTO 0); -- pulses_p
32     probe2 : IN STD_LOGIC_VECTOR(5 DOWNTO 0); -- count
33     probe3 : IN STD_LOGIC_VECTOR(0 DOWNTO 0); -- done
34     probe4 : IN STD_LOGIC_VECTOR(2 DOWNTO 0) -- state
35 );
36 END COMPONENT ;
37
38 signal pulses_p : std_logic;
39 signal done      : std_logic;
40 signal count     : unsigned(5 downto 0);
41 type state is (s_idle, s_count, s_led); -- idle
42 -- [falling pulses]
43 -- counting
44 -- [rising pulses]
45 -- led
```

```

46 signal state_fsm : state;
47
48 begin
49
50 p_fsm : process(clk, rst, pulses_in) is
51 variable cnt : integer;
52 begin
53     if rst = '1' then
54         state_fsm <= s_idle;
55         cnt := 0;
56     elsif rising_edge(clk) then
57         pulses_p <= pulses_in;
58
59         case state_fsm is
60
61         when s_idle =>
62             if pulses_in = '0' and pulses_p = '1' then -- simulate falling_edge(pulses_in)
63                 state_fsm <= s_count;
64             else
65                 state_fsm <= s_idle;
66             end if;
67             cnt := 0;
68             count <= to_unsigned(0, 6);
69             done <= '0';
70
71         when s_count =>
72             if pulses_in = '1' and pulses_p = '0' then -- simulate rising_edge(pulses_in)
73                 state_fsm <= s_led;
74             else
75                 state_fsm <= s_count;
76             end if;
77             count <= count + 1;
78
79         when s_led =>
80             if cnt < DONE_TIME - 1 then
81                 cnt := cnt + 1;
82                 state_fsm <= s_led;
83             else
84                 state_fsm <= s_idle;
85             end if;
86             done <= '1';
87
88         end case;
89
90     end if;
91
92 end process;
93
94 count_out <= count;
95 done_out <= done;
96
97 ila : ila_1
98     PORT MAP (
99         clk => clk,
100         probe0(0) => pulses_in,
101         probe1(0) => pulses_p,
102         probe2 => std_logic_vector(count),
103         probe3(0) => done,

```

```

104         probe4    => std_logic_vector(to_unsigned(state'pos(state_fsm),3))
105     );
106
107 end Behavioral;

```

2 Screenshot of ILA

 


Figura 1: Screenshot of ILA triggered in the rising edge of the done_out signal. The count and state_fsm signals are represented as Unsigned